


## EE610A: Analog VLSI Circuits

### Project / Simulation Assignment

**Submitted by : Rahul Kumar Gupta**  
**(21204408)**

## Specifications:

Input stage	VDD	CL	Loop gain (min)	−3dB Bandwidth of V0/Vi (min)	CMRR(@dc)
NMOS	1.8V	10pF	40 dB	100MHz	80dB

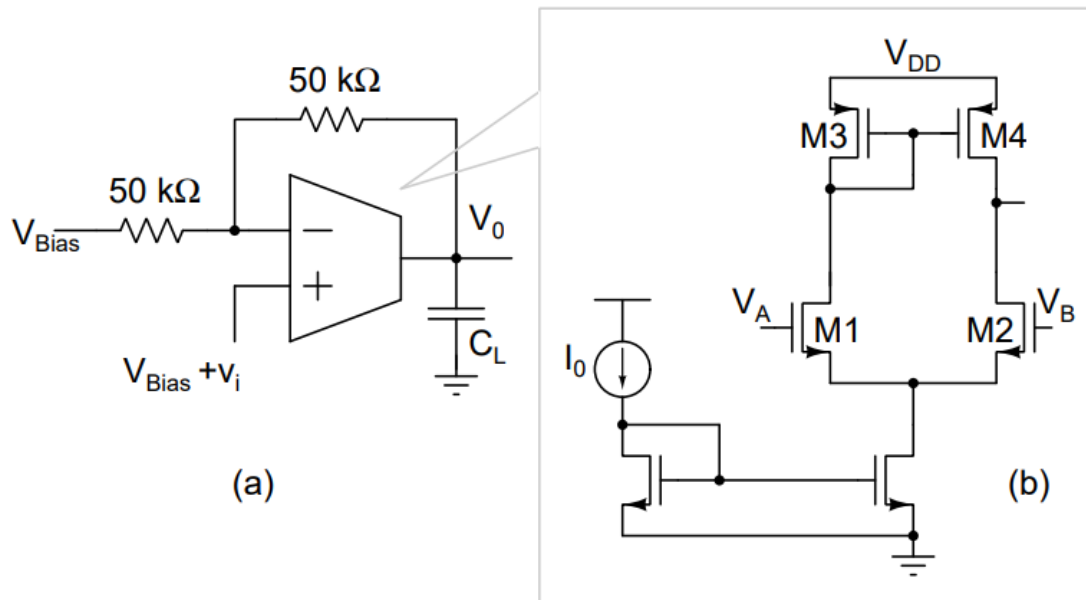

\*Given prototype

Fig. 1. (a) Top level of the opamp. (b) Prototype internal schematic (without zero cancelling resistor). (c) CMFB of first stage. (d) CMFB of second stage.

## DESIGN METHODOLOGY

1. At first, I designed and tried to achieve the specifications by a simple Differential Amplifier structure as provided in the prototype schematic.
2. With theoretical calculations, the prototype circuit had the  $w_{u,loop}$  at  $g_m/2\pi C_L$  ie. 100MHz(as per the specs)  
 $C_L = 10\text{pF}(\text{fixed})$   
 $g_m = 2\pi \text{ mS}$
3. Since the specifications were not met with that design( even after bringing  $g_m$  to the desired value), I switched to telescopic cascode structure to increase  $R_{out}$  in order to achieve a high gain.
4. Also I used the below mentioned three relations to tweak the circuit and achieve the mentioned specifications.


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I}$$

$$\frac{g_m}{g_{Ds}} \propto \sqrt{\frac{WL}{I}}$$

$$V_{ov} = \sqrt{\frac{2I}{\mu_n C_{ox} \frac{W}{L}}}$$

5. At first I tried to achieve the desired  $g_m$  value using the first relation and then I tried to get a high gain while keeping the  $g_m$  almost constant.

## Design

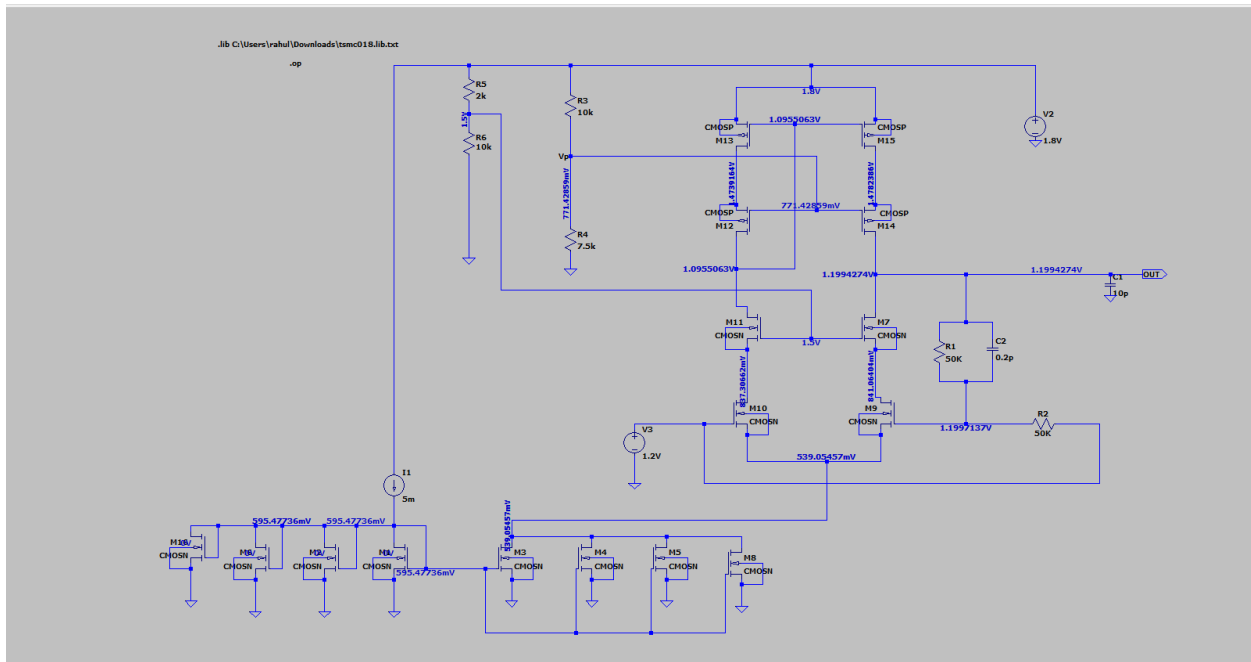

6. I also had to make two changes:

i) In the current mirror pulling down current, I had to increase the W/L of the transistors in order to match their Drain and Gate voltages → for better current mirroring.

In order to keep the NMOS transistors all the same, I added more NMOS transistors and connected them in parallel.

ii) In the feedback path, I added a Capacitor to introduce a pole.

It was done to **cancel** the zero which affected the  $V_o/V_i$  plot at high frequencies.

The value of the capacitor was determined by approximate analysis and simulations.

Name:	m15	m14	m13	m12	m16
Model:	cmosp	cmosp	cmosp	cmosp	cmosn
Id:	-2.48e-03	-2.48e-03	-2.48e-03	-2.48e-03	1.25e-03
Vgs:	-7.04e-01	-7.07e-01	-7.04e-01	-7.02e-01	5.95e-01
Vds:	-3.22e-01	-2.79e-01	-3.26e-01	-3.78e-01	5.95e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	-4.56e-01	-4.56e-01	-4.56e-01	-4.56e-01	4.64e-01
Vdsat:	-2.02e-01	-2.04e-01	-2.02e-01	-2.01e-01	1.10e-01
Gm:	1.81e-02	1.77e-02	1.81e-02	1.84e-02	1.68e-02
Gds:	8.23e-04	1.15e-03	8.02e-04	6.15e-04	1.99e-04
Gmb:	5.61e-03	5.51e-03	5.62e-03	5.69e-03	4.58e-03
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	2.70e-13	2.70e-13	2.70e-13	2.70e-13	1.48e-13
Cgdov:	2.70e-13	2.70e-13	2.70e-13	2.70e-13	1.48e-13
Cgbov:	3.01e-19	3.01e-19	3.01e-19	3.01e-19	3.26e-19


Name:	m11	m10	m9	m7	m3
Model:	cmosn	cmosn	cmosn	cmosn	cmosn
Id:	2.48e-03	2.48e-03	2.48e-03	2.48e-03	1.24e-03
Vgs:	6.63e-01	6.61e-01	6.61e-01	6.59e-01	5.95e-01
Vds:	2.58e-01	2.98e-01	3.02e-01	3.58e-01	5.39e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	4.66e-01	4.66e-01	4.66e-01	4.65e-01	4.64e-01
Vdsat:	1.48e-01	1.47e-01	1.47e-01	1.46e-01	1.10e-01
Gm:	2.32e-02	2.36e-02	2.36e-02	2.39e-02	1.67e-02
Gds:	1.20e-03	8.76e-04	8.53e-04	6.25e-04	2.10e-04
Gmb:	6.28e-03	6.38e-03	6.38e-03	6.46e-03	4.55e-03
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	1.48e-13	1.48e-13	1.48e-13	1.48e-13	1.48e-13
Cgdov:	1.48e-13	1.48e-13	1.48e-13	1.48e-13	1.48e-13
Cgbov:	3.26e-19	3.26e-19	3.26e-19	3.26e-19	3.26e-19

Name: m1  
 Model: cmosn  
 Id: 1.25e-03  
 Vgs: 5.95e-01  
 Vds: 5.95e-01  
 Vbs: 0.00e+00  
 Vth: 4.64e-01  
 Vdsat: 1.10e-01  
 Gm: 1.68e-02  
 Gds: 1.99e-04  
 Gmb: 4.58e-03  
 Cbd: 0.00e+00  
 Cbs: 0.00e+00  
 Cgsov: 1.48e-13  
 Cgdov: 1.48e-13  
 Cgbov: 3.26e-19

Name:	m8	m6	m5	m4	m2
Model:	cmosn	cmosn	cmosn	cmosn	cmosn
Id:	1.24e-03	1.25e-03	1.24e-03	1.24e-03	1.25e-03
Vgs:	5.95e-01	5.95e-01	5.95e-01	5.95e-01	5.95e-01
Vds:	5.39e-01	5.95e-01	5.39e-01	5.39e-01	5.95e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	4.64e-01	4.64e-01	4.64e-01	4.64e-01	4.64e-01
Vdsat:	1.10e-01	1.10e-01	1.10e-01	1.10e-01	1.10e-01
Gm:	1.67e-02	1.68e-02	1.67e-02	1.67e-02	1.68e-02
Gds:	2.10e-04	1.99e-04	2.10e-04	2.10e-04	1.99e-04
Gmb:	4.55e-03	4.58e-03	4.55e-03	4.55e-03	4.58e-03
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	1.48e-13	1.48e-13	1.48e-13	1.48e-13	1.48e-13
Cgdov:	1.48e-13	1.48e-13	1.48e-13	1.48e-13	1.48e-13
Cgbov:	3.26e-19	3.26e-19	3.26e-19	3.26e-19	3.26e-19

Following are the plots obtained at room temp.


## 1. Open Loop Gain and Phase

 

- Open Loop Gain obtained = 50.69 dB


## 2. Closed Loop Gain and Phase

→  $V_o/V_i$  plot

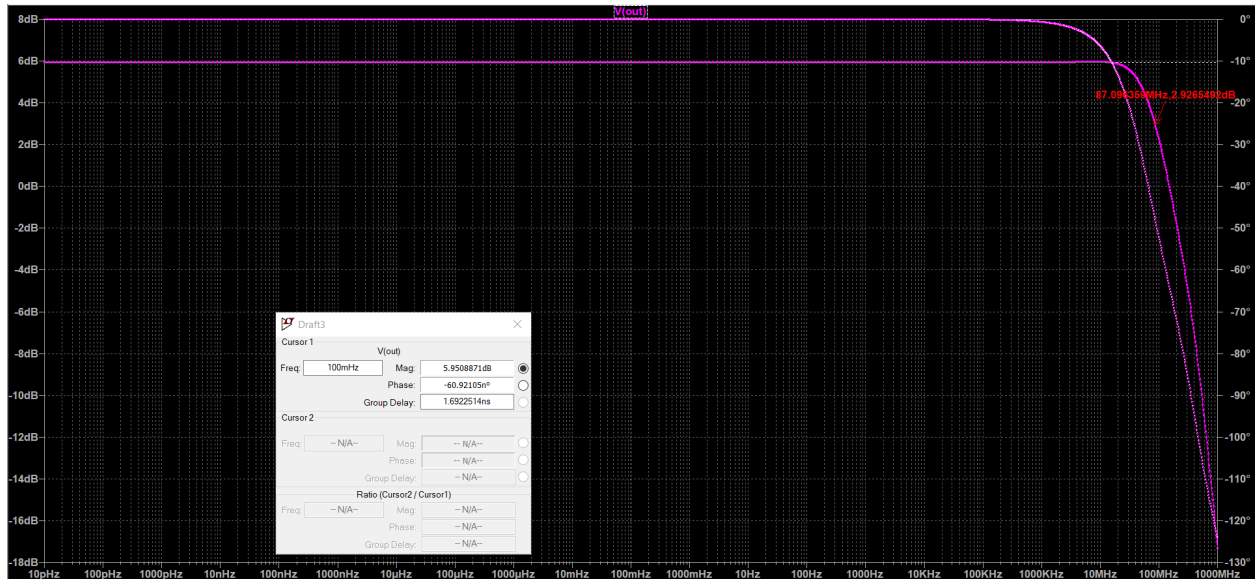

- **Closed Loop Gain obtained = 5.95 dB**
- **-3dB bandwidth = 87.09MHz**

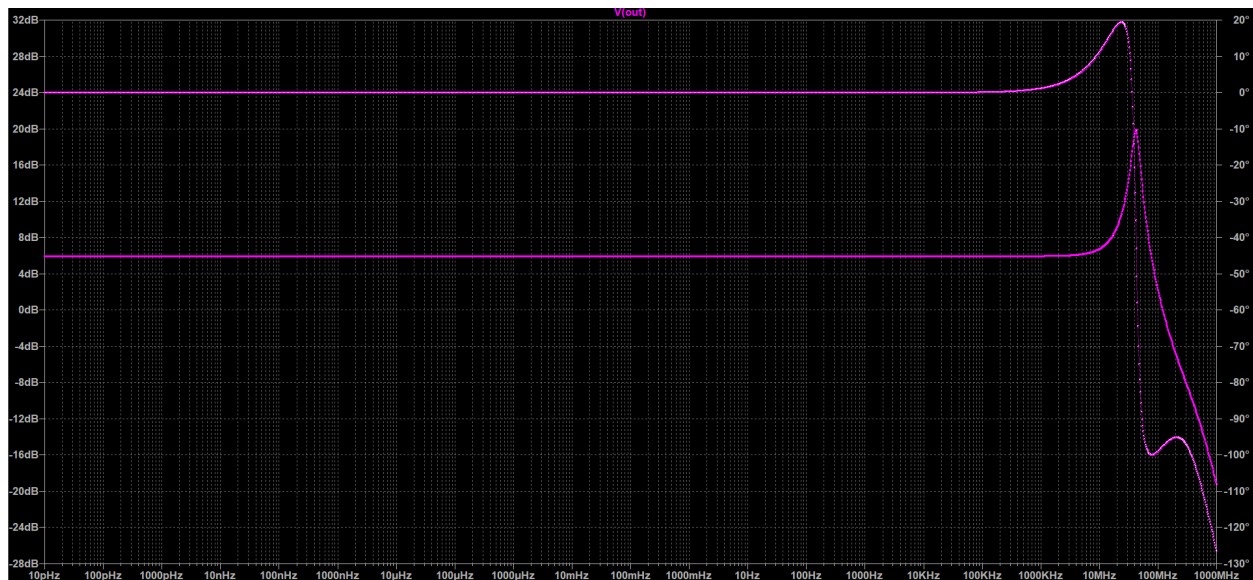
-3dB bandwidth is reduced in my design due to the addition of a pole. I added that pole (with cap. C2 in the circuit) in order to cancel the effect of a zero showing up at higher frequencies.



The above curve shows  $V_o/V_i$  without adding a pole.

- Loop Gain = Open Loop Gain - Closed Loop Gain (in dB)
- Therefore, **Loop Gain = 44.7 dB** (verified by “Big inductor” method in LTspice)

 3. Transient response of the non inverting amplifier with a 0.01 step input at  $v_i$ .



$V_{out}$  reaches 1.219V at steady state.

Ideal  $V_{out} = 1.2 + 2 \cdot 0.01 \text{ V} = 1.22 \text{ V}$


$$e_{ss} = 1.22 - 1.219$$

$$e_{ss} = 0.001 \text{ V}$$



 
4. Transient response of the non inverting amplifier with  $v_i = 150\text{mV}(\cos(w_{3\text{dB}}t))$

As per my design  $w_{3\text{dB}} = 87.09\text{MHz}$



Green→ input Blue→output

 5. Transient response of the non inverting amplifier with  $v_i = 150\text{mV}(\cos(w_{3\text{dB}}t/10))$




Green→ input Blue→output

 6. Difference between input voltages for  $v_i = 150\text{mV}(\cos(w_{3\text{dB}}t))$

→  $V1-V2 = 58 \text{ mV}$  (approx)

→  $V1-V2 = 0 \text{ mV}$  due to virtual short (theoretically)




\*Difference is shown by the red curve

 7. Difference between input voltages for  $v_i = 150\text{mV}(\cos(w_{3\text{dB}}t/10))$

→  $V1-V2 = 11.35\text{mV}(\text{max})$

→  $V1-V2 = 0 \text{ mV}(\text{theoretically})$




\*Difference is shown by the red curve

## 8. Common Mode Rejection Ratio


→ Plotting Common Mode Gain

**$A_{cm} = -38.82 \text{ dB}$**

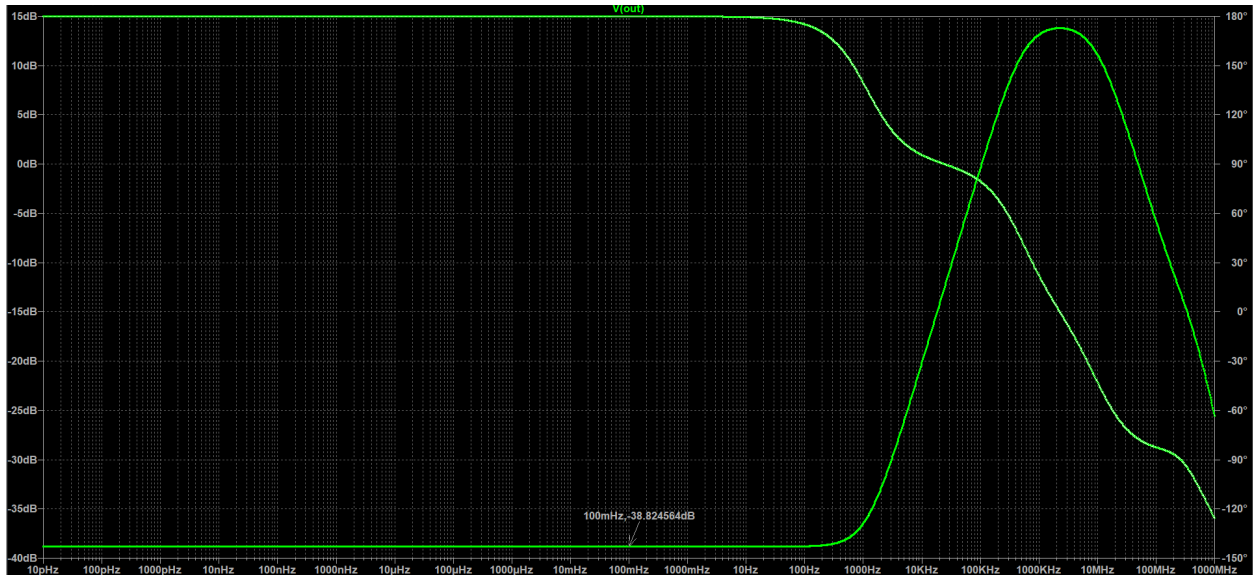

→ Plotting Differential Gain

**$A_d = 50.69 \text{ dB}$**

 


$$\text{CMRR} = A_d - A_{CM} = 89.51 \text{ dB}$$

## 9. ICMR calculation

The design approach for ICMR is as follows: -

 
- 1) Run a low frequency analysis on the Diff Amp circuit with different  $V_{CM}$  values.
- 2) Using parametric analysis, the values of  $V_{CM}$  will be varied in steps of 0.3V ranging from 0 to 1.8V.

Using transient analysis, observe the gain for various  $V_{CM}$  values and calculate  $ICMR^+$  and  $ICMR^-$  from a plot of Gain vs  $V_{cm}$ .



\* $V_{out}$  plots for different values of  $V_{CM}$ .

### Plot of Gain (dB) vs $V_{CM}$ (mV)

 

- In the above plot it can be seen that Gain is almost constant between 600mV and 1.2V.
- Therefore, an estimate of ICMR can be determined

$$\text{ICMR}^+ = 1.2\text{V}$$

$$\text{ICMR}^- = 0.6\text{V}$$

10. Below are the plots for different temperature values

### 10.1 Closed Loop Gain and Phase



## 10.2 Open Loop Gain and Phase



